

ECE315 Lab 2 Winter 2017 Schematic  
 Please use VCC=3.3 Volts for both the encoder and the multiplexor  
 All grounds need to be common  
 Pins for the Tutorial and Lab 1 are included for information only

